

Hardware Description Languages

- **Verilog** – created in 1984 by Philip Moorby of Gateway Design Automation (merged with Cadence)
 - IEEE Standard 1364-1995/2001/2005
 - Based on the C language
 - Verilog-AMS – analog & mixed-signal extensions
 - IEEE Std. 1800-2012 “System Verilog” – Unified hardware design, spec, verification
- **VHDL** = VHSIC Hardware Description Language
 - (VHSIC = Very High Speed Integrated Circuits)
 - Developed by DOD from 1983 – based on ADA language
 - IEEE Standard 1076-1987/1993/2002/2008
 - VHDL-AMS supports analog & mixed-signal extensions

HDLs in Digital System Design

- **Model** and **document** digital systems
 - **Behavioral** model
 - describes I/O responses & behavior of design
 - **Register Transfer Level (RTL)** model
 - data flow description at the register level
 - **Structural** model
 - components and their interconnections (netlist)
 - hierarchical designs
- **Simulation** to verify circuit/system design
- **Synthesis** of circuits from HDL models
 - using components from a technology library
 - output is primitive cell-level netlist (gates, flip flops, etc.)

Verilog Modules

The **module** is the basic Verilog building block

```
Module name  List of I/O signals (ports)
    ↓        ↓
module small_block (a, b, c, o1, o2);
    input a, b, c;      } I/O port direction declarations
    output o1, o2;      }
    wire s;             ← Internal wire (net) declarations

    assign o1 = s | c;    // OR operation
    assign s = a & b;     // AND operation
    assign o2 = s ^ c;    // XOR operation
endmodule              } Logic functions

(Keywords in bold)
```

Lexical conventions

- **Whitespaces** include space, tab, and newline
- **Comments** use same format as C and C++:
 - // this is a one line comment to the end of line*
 - /* this is another single line comment */*
 - /* this is a multiple
line comment */*
- **Identifiers**: any sequence of
 - letters (a-z, A-Z), digits (0-9), \$ (dollar sign) and _ (underscore).
 - the first character must be a letter or underscore*Identifier_15, adder_register, AdderRegister*
- Verilog is **case sensitive** (VHDL is case insensitive)
Bob, BOB, bob // three different identifiers in Verilog
- **Semicolons** are statement delimiters; **Commas** are list separators

Verilog module structure

module module_name (port list);

port and net declarations (IO plus wires and regs for internal nodes)

input, **output**, **inout** - directions of ports in the list

wire: internal “net” - combinational logic (needs a driver)

reg: data storage element (holds a value – acts as a “variable”)

parameter: an identifier representing a constant


functional description

endmodule

Module “ports”

- A port is a module input, output or both
 
```
module full_adder (ai, bi, cini, si, couti);  
    input ai, bi, cini;      //declare direction and type  
    output si, couti;        //default type is wire
```



- Verilog 2001: Signal port direction and data type can be combined

```
module dff (d, clk, q, qbar); //port list  
    input d, clk;  
    output reg q, qbar;      // direction and type
```

- Verilog 2001: Can include port direction and data type in the port list (ANSI C format)


```
module dff (input d,  
            input clk,  
            output reg q, qbar);
```

Data types

- **Nets** **connect** components and are continuously assigned values
 - **wire** is main net type (**tri** also used, and is identical)
- **Variables** store values between assignments
 - **reg** is main variable type
 - Also **integer**, **real**, **time** variables
- **Scalar** is a single value (usually one bit)
- **Vector** is a set of values of a given type
 - **reg** [7:0] v1,v2; //8-bit vectors, MSB is highest bit #
 - **wire** [1:4] v3; //4-bit vector, MSB is lowest bit #
 - **reg** [31:0] memory [0:127]; //array of 128 32-bit values
 - {v1,v2} // 16-bit vector: concatenate bits/vectors into larger vector

Logic values

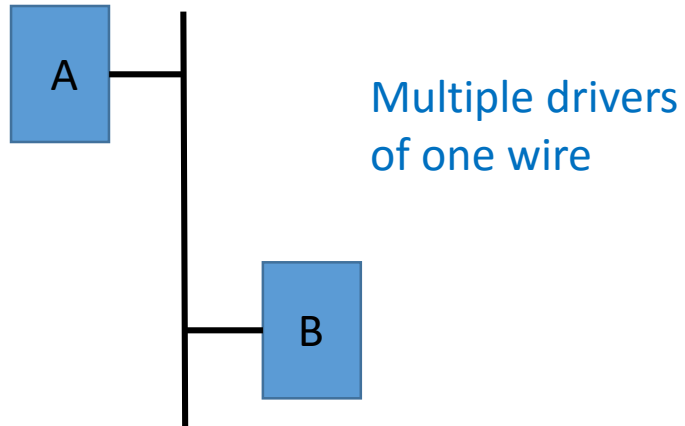- **Logic values:** 0, 1, x, z x = undefined state
z = tri-state/floating/high impedance



		B			
wire		0	1	x	z
A	0	0	x	x	0
	1	x	1	x	1
	x	x	x	x	x
	z	0	1	x	z
		State of the net			

Analagous to VHDL
std_logic values
'0' '1' 'X' 'Z'

Numeric Constants

- **Numbers/Vectors:** (bit width)'(radix)(digits)

Verilog:

4'b1010

12'ha5c

6'o71

8'd255

255

16'bZ

6'h5A

10'h55

10'sh55

-16'd55

VHDL:

"1010" or B"1010"

X"0a5c"

O"71"

255

255

x"ZZZZ"

x"5A"

Note:

4-bit binary value

12-bit hexadecimal value

6-bit octal value

8-bit decimal value

32-bit decimal value (default)

16-bit floating value

6-bit value, upper bits truncated

10-bit value, zero fill left bits

10-bit signed-extended value

16-bit negative decimal (-55)

Equating symbols to constants

- Use **define** to create **global** constants (*across modules*)

```
'define WIDTH 128
'define GND 0
module (input [WIDTH-1:0] dbus)
...

```

- Use **parameter** to create **local** constants (*within a module*)

```
module StateMachine ( )
    parameter StateA = 3'b000; parameter StateB = 3'b001;
    ...
    always @(posedge clock)
        begin
            if (state == StateA)
                state <= StateB;    //state transition
        end
endmodule

```


Verilog module examples

// Structural model of a full adder

```
module fulladder (si, couti, ai, bi, cini);  
    input ai, bi, cini;  
    output si, couti;  
    wire d,e,f,g;  
    xor (d, ai, bi);  
    xor (si, d, cini);  
    and (e, ai, bi);  
    and (f, ai, cini);  
    and (g, bi, cini);  
    or (couti, e, f, g);  
endmodule
```

Gate
instances

Continuous
driving of a
net

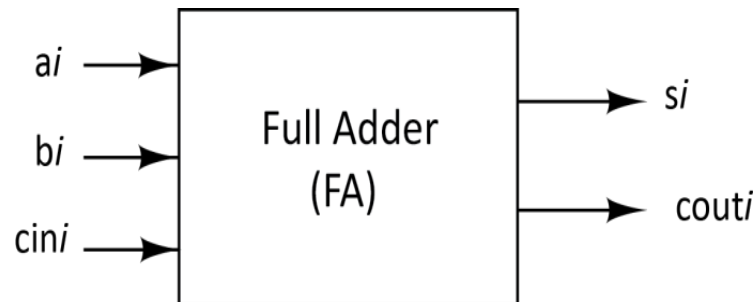

// Dataflow model of a full adder

```
module fulladder (si, couti, ai, bi, cini);  
    input ai, bi, cini;  
    output si, couti;  
    assign si = ai ^ bi ^ cini;  
    // ^ is the XOR operator in Verilog  
    assign couti = ai & bi | ai & cini | bi & cini;  
    // & is the AND operator and | is OR  
endmodule
```

// Behavioral model of a full adder

```
module fulladder (si, couti, ai, bi, cini);  
    input ai, bi, cini;  
    output si, couti;  
    assign {couti,si} = ai + bi + cini;  
endmodule
```

Operators (in *increasing* order of precedence*):

		logical OR			
	&&	logical AND			
		bitwise OR	~	bitwise NOR	
	^	bitwise XOR	~^	bitwise XNOR	
	&	bitwise AND	~&	bitwise NAND	
	==	logical equality	!=	logical inequality	
	<	less than	<=	less than or equal	
<i>also</i>	>	greater than	>=	greater than or equal	
	<<	shift left	>>	shift right	
	+	addition	-	subtraction	
	*	multiply	/	divide	% modulus

*Note that: $A \& B \mid C \& D$ is equivalent to: $(A \& B) \mid (C \& D)$

$A * B + C * D$ is equivalent to: $(A * B) + (C * D)$

Preferred forms - emphasizing precedence

Unary operators:

!	logical negation
~	bitwise negation
&	reduction AND
~&	reduction NAND
	reduction OR
~	reduction NOR
^	reduction XOR
~^	reduction XNOR

Examples:

~4'b0101 is 4'b1010

& 4'b1111 is 1'b1

~& 4'b1111 is 1'b0

| 4'b0000 is 1'b0

~| 4'b0000 is 1'b1

^ 4'b0101 is 1'b0

~^ 4'b0101 is 1'b1

***reduction** operator
is applied to bits of a
vector, returning a
one-bit result*

Combining statements

// Wire declaration and subsequent signal assignment

```
wire a;
```

```
assign a = b | (c & d);
```

// Equivalent to:

```
wire a = b | (c & d);
```

Examples: 2-to-1 multiplexer

// function modeled by its “behavior”

```
module MUX2 (A,B,S,Z);  
input A,B,S;           //input ports  
output Z;              //output port  
always                 //evaluate block continuously  
begin  
    if (S == 0) Z = A;  //select input A  
    else       Z = B;  //select input B  
end  
endmodule
```

A, B, Z could
also be **vectors**
(of equal # bits)

// function modeled as a logic expression

```
module MUX2 (A,B,S,Z);  
input A,B,S;           //input ports  
output Z;              //output port  
    assign Z = (~S & A) | (S & B); //continuous evaluation  
endmodule
```

Using conditional operator:

assign Z = (S == 0) ? A : B;

True/false
condition

if true : if false

Multi-bit signals (vectors)

// Example: 2-to-1 MUX with 4-bit input/output vectors

```
module MUX2ARR(A,B,S,Z);  
  input [3:0] A,B;    // whitespace before & after array declaration  
  input S;  
  output [3:0] Z;     // little-endian form, MSB = bit 3 (left-most)  
  reg [0:3] G;        // big-endian form, MSB = bit 0 (left-most)  
  always  
    begin  
      if (S == 0) G = A;    //Select 4-bit A as value of G  
      else      G = B;    //Select 4-bit B as value of G  
    end  
  assign Z = G;  
endmodule
```

A,B,Z,G analagous to
VHDL std_logic_vector

Examples: 4-to-1 multiplexer

// function modeled by its "behavior"

```
module MUX2 (A,B,C,D,S,Z1,Z2);
```

```
input A,B,C,D;
```

//mux inputs

```
input [1:0] S;
```

//mux select inputs

```
output Z;
```

//mux output

```
always //evaluate block whenever there are changes in S,A,B,C,D
```

```
begin //if-else form
```

```
if (S == 2'b00) Z1 = A;
```

//select input A for S=00

```
else if (S == 2'b01) Z1 = B;
```

//select input B for S=01

```
else if (S == 2'b10) Z1 = C;
```

//select input C for S=10

```
else if (S == 2'b11) Z1 = D;
```

//select input D for S=11

```
else Z1 = x;
```

//otherwise unknown output

```
end
```

//assign statement using the conditional operator (in lieu of always block)

```
assign Z2 = (S == 2'b00) ? A:
```

//select A for S=00

```
(S == 2'b01) ? B:
```

//select B for S=01

```
(S == 2'b10) ? C:
```

//select C for S=10

```
(S == 2'b11) ? D:
```

//select D for S=11

```
x;
```

//otherwise default to x

```
endmodule
```

//equivalent case statement form

```
case (S)
```

```
2'b00: Z1 = A;
```

```
2'b01: Z1 = B;
```

```
2'b10: Z1 = C;
```

```
2'b11: Z1 = D;
```

```
default: Z1 = x;
```

```
endcase
```

Synthesis may insert latches
when defaults not specified.

Hierarchical structure of 4-to-1 MUX (using the previous 2-to-1 MUX)

```
module MUX4 (A,B,c,d,S0,S1,Z);
```

```
  input A,B,c,d,S0,S1;
```

```
  output Z;
```

```
  wire z1,z2;
```

```
  MUX2 M1(A,B,S0,z1);
```

```
  MUX2 M2(c,d,S0,z2);
```

```
  MUX2 M3(.S(S1), .Z(Z), .A(z1),.B(z2));
```


```
//instance M1 of MUX2
```

```
//instance M2 of MUX2
```

```
//connect signal to port: .port(signal)
```

```
// more descriptive, less error-prone
```

```
endmodule
```

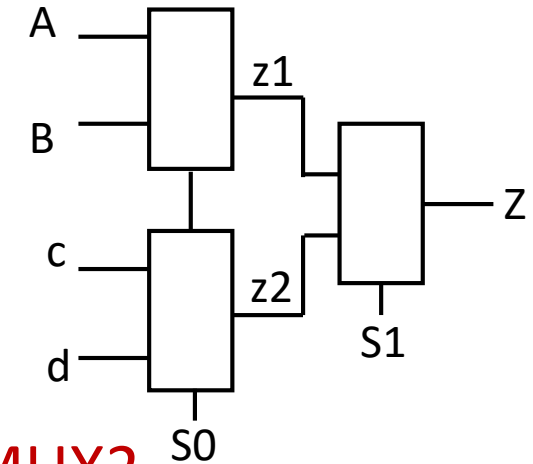

Define MUX2 module in Verilog source before compiling MUX4 module

Procedural statements and blocks

- A **procedure** can be an: **always** block, **initial** block, **function**, **task**
 - Define functionality in an algorithmic manner
 - Insert multiple procedural statements between **begin** .. **end** keywords
- A **block** contains one or more “procedural statements”
 - **initial** block
 - Executes immediately at start of simulation
 - Executes one time only
 - Used primarily to initialize **simulation** values (rather than for synthesis)
 - **always** block
 - Executes as an “infinite loop”
 - Executes immediately at start of simulation
 - Executes again whenever “enabled”
 - Enablement can result from time delay, signal change, signal state, etc.

See previous adder/multiplexer examples.

Example: generating a clock

```
wire clk;
initial //execute once – at start of simulation
    begin
        clk <= 0;           //initial state of clk
        reset <= 0;        //initial state of reset line
        #10 reset <= 1;     //delay until time 10, and set reset to 1
        #10 reset <= 0;     //delay until time 20, and set reset back to 0
    end
always //execute as infinite loop, beginning at start of simulation
    begin
        #10 clk <= ~clk;    //suspend loop for 10 time units, toggle clk, and repeat
    end
end
```

If a block contains a single procedural statement, begin-end can be omitted.

ELEC 4200 Lab 2: Binary to Seven-Segment Display Driver

```
module bin_2_7seg (seg7, hexval);  
  input [2:0] hexval;  
  output [6:0] seg7;  
  reg [6:0] seg7;  
  
  always @(hexval) begin //any change in hexval initiates execution  
    case (hexval)  
      3'b000: seg7 = 7'b1000000; //0  
      3'b001: seg7 = 7'b1111001; //1  
      3'b010: seg7 = 7'b0100100; //2  
      3'b011: seg7 = 7'b0110000; //3  
      3'b100: seg7 = 7'b0011001; //4  
      3'b101: seg7 = 7'b0010010; //5  
      3'b110: seg7 = 7'b0000010; //6  
      3'b111: seg7 = 7'b1111000; //7  
    endcase  
  end  
endmodule
```

Enabling a procedural block with a clock

@ (posedge CLK) wait for rising edge of CLK (0->1, 0->X, X->1)
@ (negedge CLK) wait for falling edge of CLK (1->0, 1->X, X->0)
@ (CLK) wait for either edge of CLK

//Example: simple rising-edge triggered flip-flop:

```
always @ (posedge CLK) //wait for rising CLK edge
begin
    Q <= D;      //Q changes on rising edge
end
```

} Analagous to VHDL
process with CLK in
sensitivity list

//Example: falling-edge triggered flip-flop with sync preset and clock enable:

```
always @ (negedge CLK)
begin
    if (PR == 1) Q <= 1;      //synchronous set
    else if (CE == 1) Q <= D;      //clock enable
end
```

DFF example – with asynchronous reset

```
module dff (q,d,clk,reset)
  input d,clk,reset;
  output q;
  reg q;           //”reg” since q stores the flip flop state
                  //can combine above two lines:  output reg q;

  always @(posedge clk or posedge reset) //sensitive to clk or reset change
    if (reset)
      q <= 1'b0;           //load prevented if reset active
    else
      q <= d;              //load if rising clk edge when reset not active
endmodule
```

DFF example – with synchronous reset

```
module dff (q,d,clk,reset)
  output reg q;           //”reg” since q stores the flip flop state
  input d, clk, reset;

  always @(posedge clk)   //sensitive to rising edge of clk
    if (reset)            //reset takes precedence over load
      q <= 1'b0;
    else                  //load if reset not active
      q <= d;
endmodule
```


DFF-based register with asynchronous reset

//Use in RTL models

```
module dreg (q,d,clk,reset)
  input clk,reset;
  input [31:0] d;           //32-bit input
  output reg [31:0] q;      //32-bit register state
  always @(posedge clk or posedge reset) //react to clk or reset change
    if (reset)              //reset takes precedence over clock
      q <= 0;               //load 32-bit constant 0
    else                    //rising clk edge while reset=0
      q <= d;               //load 32-bit input
endmodule
```

D latch (level sensitive)

// q and d could also be vectors

```
module d_latch (q,d,en)
```

```
    input d,en;
```

```
    output reg q;
```

//q output holds a value

```
    always @(en or d)
```

//wait until en or d change

```
        if (en) q <= d;
```

//q becomes d while en=1

```
endmodule
```

Sensitivity list for combinational logic

// function modeled by its “behavior”

```
module MUX2 (A,B,S,Z);
```

```
input A,B,S;           //input ports
```

```
output reg Z;          //output port
```

```
always @(S or A or B)  //evaluate block on any change in S,A,B
```

```
begin
```

```
    if (S == 0) Z = A;    //select input A
```

```
    else      Z = B;      //select input B
```

```
end
```

```
endmodule
```

All inputs to
the combinational
logic function



Alternative:

always @()*

Where * indicates any
signal that might affect
another within this block.

Timing control and delays**

`'timescale 1ns/10ps` `//time units/precision (s,ns,ps,fs), multiplier=1,10,100`

Intra-assignment:

<code>x = #5 y;</code>	<code>//Equivalent to the following</code>
<code> hold = y;</code>	<code>//capture y at t = 0</code>
<code> #5;</code>	<code>//delay until t = 5</code>
<code> x = hold;</code>	<code>//update x</code>

Delayed assignment:

<code>#5 x = y;</code>	<code>//Equivalent to the following</code>
<code> #5;</code>	<code>//delay from t = 0 until t = 5</code>
<code> x = y;</code>	<code>//copy value of y to x</code>

**** *Delays are ignored by synthesis tools***

Blocking vs non-blocking assignments

- **Blocking** statements ($x = y;$)
 - Executed in order listed, **delaying execution of next statement as specified**
 - Effects of one statement take effect before next statement executed
 - Will not block execution of statements in parallel blocks
 - Use for modeling **combinational** logic
- **Non-blocking** statements ($x \leq y;$)
 - **Schedule** assignments without blocking other statements
 - Execute next statement without waiting for first statement to execute
 - Use for modeling **sequential** logic

//Blocking example

```
A = B;      //block until after A changes  
C = A + 1;  //use "new" A value from above
```

//Non-blocking example

```
A <= B;     //schedule A change and continue  
C <= A + 1; //use "old" A value – not the new one
```

Blocking vs non-blocking examples

// Blocking example

```
x = 0;           // x changes at t = 0
a = 1;           // a changes at t = 0
#10 c = 3;        // delay until t=10, then c changes
#15 d = 4;        // delay until t=25, then d changes
e = 5;           // e changes at t = 25
```

//Non-blocking example

```
x = 0;           //execute at t = 0
a = 1;           //execute at t = 0
c <= #15 3;       //evaluate at t = 0, schedule c to change at t = 15
d <= #10 4;       //evaluate at t = 0, schedule d to change at t = 10
c <= c + 1;       //evaluate at t = 0, schedule c to change at t = 0
```

Example of blocking/non-blocking delays

initial begin

```
a = 1; b = 0; //block until after change at t=0
#1 b = 1;     //delay until t=1; then block until b=1
c = #1 1;     //block until t=2, c=val from t=1
#1;           //delay to t=3
d = 1;        //block until change at t=3
e <= #1 1;    //non-blocking, update e at t=4
#1 f <= 1;    //delay to t=4, non-blocking f update
g <= 1;       //still t=4, non-blocking g update
```

end

Results:

t	a	b	c	d	e	f	g
0	1	0	x	x	x	x	x
1	1	1	x	x	x	x	x
2	1	1	1	x	x	x	x
3	1	1	1	1	x	x	x
4	1	1	1	1	1	1	1

Example

- **Blocking: (a-b end up with same value – race condition)**

```
always @(posedge clock)
```

```
    a = b;                                //change a NOW
```

```
always @(posedge clock)
```

```
    b = a;                                //change b to new a value
```


- **Non-blocking: (a-b swap values)**

```
always @(posedge clock)
```


```
    a <= b;                                //read b at t=0, schedule a to change
```

```
always @(posedge clock)
```
 
```
    b <= a;                                //read a at t=0, schedule b to change
```



Non-blocking examples

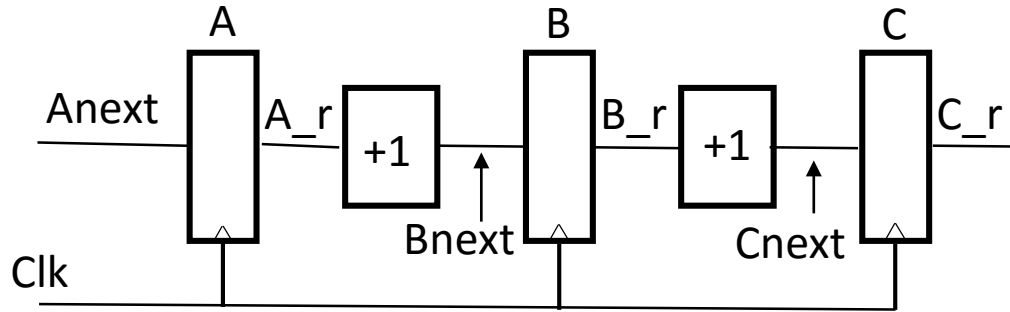

```
// Registers react to clock concurrently
// Adders modeled as combinational logic
wire Anext, Bnext, Cnext;
reg A_r, B_r, C_r;
always @(posedge Clk) begin
    A_r <= Anext; //load FFs
    B_r <= Bnext; //after delay
    C_r <= Cnext;
end;
//Comb logic with blocking stmts
assign Bnext = A_r + 1;
assign Cnext = B_r + 1;
```

```
// Registers react to clock concurrently
// "old values" at rising clock time, before outputs change
wire Anext;
reg A_r, B_r, C_r;
always @(posedge Clk) begin
    A_r <= Anext; //A_r to change later
    B_r <= A_r + 1; //use "old" A_r
    C_r <= B_r + 1; //use "old" B_r
end;
```

Arithmetic operations for RTL modeling

- Verilog recognizes standard arithmetic operators
- Synthesis tools will generate arithmetic circuits

```
module Adder_8 (A, B, Z, Cin, Cout);  
    input [7:0] A, B;           //8-bit inputs  
    input Cin;                  //carry input bit  
    output [7:0] Z;             //8-bit sum  
    output Cout;                //carry output bit  
    assign {Cout, Z} = A + B + Cin; //extra output bit for carry  
endmodule
```

The size of the operation is that of the largest operand (input or output).
In this example, the result is 9 bits, which is the size of {Cout,Z}.

Alternate adder example

```
module Adder_16 (A, B, Z, Cin, Cout);  
    input [31:0] A, B;           //32-bit inputs  
    input Cin;                   //carry input bit  
    output [31:0] Z;             //32-bit sum  
    output Cout;                 //carry output bit  
    wire [33:0] Temp;           //34-bit temporary result  
    assign Temp = {1'b0,A,Cin} + {1'b0,B,1'b1}; //1 added to bit 1 if Cin=1  
    assign {Cout, Z} = Temp[33:1]; //Cout=bit 33, Sum=bits 32:1  
endmodule
```

Optimizing circuits (1)

//synthesis tool infers two adders from the following

```
module Add1 (sel, a, b, c, d, y);  
  input a, b, c, d, sel; output reg y;  
  always @(sel or a or b or c or d) begin  
    if (sel == 0)    //mux selects output  
      y <= a + b;    //adder 1  
    else  
      y <= c + d;    //adder 2  
  end  
endmodule
```

Optimizing circuits (2)

//synthesis tool infers a single adder from the following

//indicate that a mux selects adder inputs

```
module Add2 (sel, a, b, c, d, y);  
  input a, b, c, d, sel; output y; reg t1, t2, y;  
  always @(sel or a or b or c or d) begin  
    if (sel == 0) //muxes select adder inputs  
      begin t1 = a; t2 = b; end  
    else  
      begin t1 = c; t2 = d; end  
    y = t1 + t2; //adder circuit  
  end  
endmodule
```

Note use of blocking statements
to ensure desired adder inputs

Conditional statements

- *if-else* constructs
 - like C, except that instead of open and close brackets { ... } use keywords *begin* ... *end* to group multiple assignments associated with a given condition
 - *begin* ... *end* are not needed for single assignments
- *case* constructs
 - similar to C switch statements, selecting one of multiple options based on values of a single selection signal
- *for* ($i = 0; i < 10; i = i + 1$) *statements*
- *repeat* (*count*) *statements* *//repeat statements “count” times*
- *while* (*abc*) *statements* *//repeat statements while abc “true” (non-0)*

if-else example: 4-to-1 multiplexer

```
module MUX4 (A,B,C,D,S0,S1,Z);  
input A,B,C,D,S0,S1;  
output Z;  
wire Z1,Z2;  
always  
    begin  
        if      ((S1 == 1'b0) && (S0 == 1'b0)) Z = A;  
        else if ((S1 == 1'b0) && (S0 == 1'b1)) Z = B;  
        else if ((S1 == 1'b1) && (S0 == 1'b0)) Z = C;  
        else                                     Z = D;  
    end  
endmodule
```

```

module tri_asgn (source, ce, wrclk, selector, result) ;
input [3:0] source ;
input ce, wrclk ;
input [1:0] selector ;
output reg result ;
reg [3:0] intreg;
tri result_int ; //tri (tri-state) is same as wire
// combine net declaration and assignment
wire [1:0] sel = selector;
// select one "intreg" bit to drive "result"
assign // (condition) ? true-result : false-result
    result_int = (sel == 2'b00) ? intreg[0] : 1'bZ ,
    result_int = (sel == 2'b01) ? intreg[1] : 1'bZ ,
    result_int = (sel == 2'b10) ? intreg[2] : 1'bZ ,
    result_int = (sel == 2'b11) ? intreg[3] : 1'bZ ;

```

Example: tri-state bus driver

```

// "if" statement
always @(posedge wrclk)
begin
    if (ce)
        begin
            intreg = source ;
            result = result_int ;
        end
    end
endmodule

```


FSM modeling styles

```

module MooreFSM (CLK,X,Z);
input CLK,X;
output Z;
reg [1:0] CS;
parameter SA = 2'b00           // define state A with binary value 00
parameter SB = 2'b01           // define state B with binary value 01
parameter SC = 2'b10           // define state C with binary value 10


```

// State transitions

```

always @ (posedge CLK)
begin
    if (CS == SA) // IF-ELSE form
    begin
        if (X == 0) CS = SC;
        else CS = SB;
    end
    else if (CS == SB)
    begin
        if (X == 0) CS = SA;
        else CS = SC;
    end
    else
    begin
        if (X == 0) CS = SB;
        else CS = SA;
    end
end
end

```

 

// Moore model output

```

always @ (CS)
begin //CASE statement form
    case (CS) // CASE (selector)
        SA: begin
            Z = 1'b0;
        end
        SB: begin
            Z = 1'b1;
        end
        SC: begin
            Z = 1'b1;
        end
    endcase
end
endmodule

```

/* ELEC 4200 Lab 4 – Moore model finite state machine */

module MooreFSM (RST, EN, Clock, OUT, C1, C0);

input RST, EN, Clock; **output** C1, C0;

output [3:0] OUT; **reg** [3:0] OUT;

parameter S0 = 4'b0001; **parameter** S1 = 4'b0010;

parameter S2 = 4'b0100; **parameter** S3 = 4'b1000;

always @(posedge Clock) **begin**

if (RST == 1) **begin**

 OUT = S0; //reset to S0

end

else if (EN == 1) **begin** //state changes

case (OUT)

 S0: OUT = S1;

 S1: OUT = S2;

 S2: OUT = S3;

 S3: OUT = S0;

endcase


end

end

assign C1 = OUT[3] | OUT[2]; //Encode outputs

assign C0 = OUT[1] | OUT[3];

endmodule

 

```
/* ELEC 4200 Lab 5 – Universal 8-bit register/counter */
```

```
module Counter(CLK, RST, CE, M, Din, Q);
```

```
  input CLK, RST, CE;
```

```
  input [1:0] M;
```

```
  input [7:0] Din;
```

```
  output reg [7:0] Q;
```

```
always @(posedge CLK) begin
```

```
  if (RST) begin
```

```
    Q = 8'h00;
```

```
    //reset
```

```
  end
```

```
  else if (CE) begin
```

```
    //clock enable
```

```
    if (M == 2'b01) Q = Q << 1; //shift
```


```
    else if (M == 2'b10) Q = Q + 1; //count
```

```
    else if (M == 2'b11) Q = Din; //load
```

```
  end
```

```
end
```

```
endmodule
```

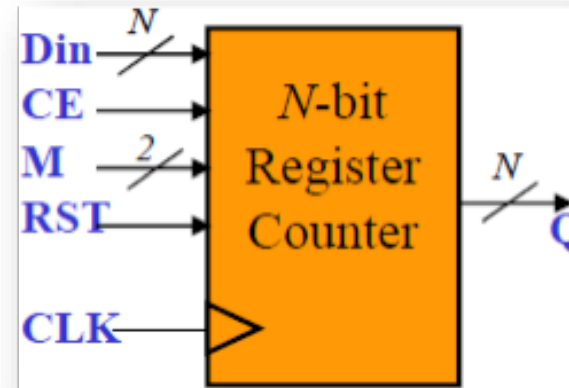

for loop – similar to C construct

// 32-bit full adder

always

begin

for (n=0; n<32; n++) **// ripple carry form**

begin

sum[n] = Ain[n] ^ Bin[n] ^ carry[n];

carry[n+1] = (Ain[n] & Bin[n]) | (Ain[n] & carry[n]) | (Bin[n] & carry[n]);

end

end

while loop – execute until while expression not true

```
reg [15:0] buffer [0:7];
integer k;
...
always @(posedge clock)
    begin
        k = 8;
        while (k)           //store data at posedge of next 8 clocks
            begin
                k = k - 1;    //copy data to words 7-0 of buffer
                @(posedge clock) buffer[k] = data;
            end
        end
    end
```

repeat loop – repeat a fixed #times


```
parameter cycles = 8;    // repeat loop counter for below
reg [15:0] buffer [0:7];
integer k;
...
always @(posedge clock)
    begin
        k = 0;
        repeat (cycles)    //store data at posedge of next 8 clocks
            begin //fill buffer words 0-7 with data
                @(posedge clock) buffer[k] = data;
                k = k + 1;
            end
        end
    end
```

Memory models

- **Memory** is an array of registers

```
reg [7:0] accumulator;           //8-bit register
reg mem1bit [ 0:1023];           //array of bits
reg [7:0] membyte [0:1023]      //array of bytes
```

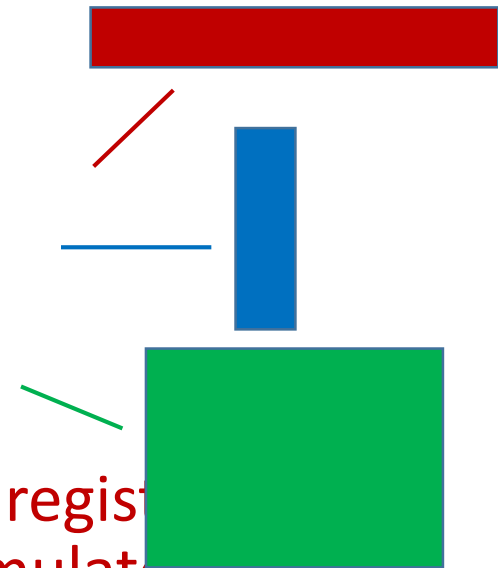mem1bit[511] - refers to one bit of memory
membyte[511] - refers to one byte of memory
accumulator[5] – refers to bit 5 of the accumulator register
accumulator[3:0] – refers to lower half of the accumulator register



- Additional dimensions: `reg [7:0] mem [0..127][0..63]`

```
/* Lab 6 - Register file */
```

```
`timescale 1ns / 1ns
```

```
module RegFile (ReadAddress, WriteAddress, WE, DataIn, DataOut);
```

```
    input [3:0] ReadAddress, WriteAddress;
```

```
    input [7:0] DataIn;
```

```
    input WE;
```

```
    output [7:0] DataOut;
```

```
    reg [7:0] RF [0:15];           //16 8-bit registers
```

```
    assign DataOut = RF[ReadAddress]; //continuous read
```


```
    always @(WE) begin
```

```
        if (WE)
```

```
            RF[WriteAddress] = DataIn; //write register
```

```
    end
```

```
endmodule
```

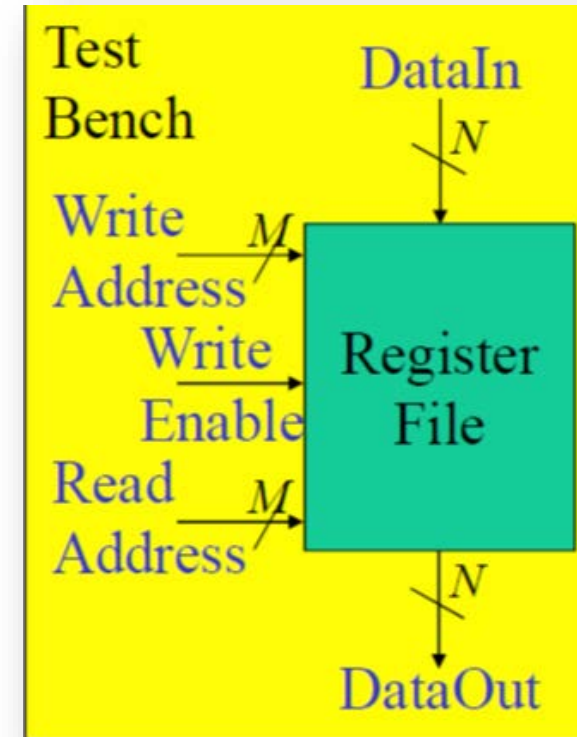


```
//-----  
// Title Lab 6 test bench : RegFile_tb  
//-----
```

```
`timescale 1ns / 1ns
```

```
module RegFile_tb;
```

```
//Internal signals declarations:
```

```
reg [3:0]ra;
```

```
reg [3:0]wa;
```

```
reg we;
```

```
reg [7:0]din;
```

```
wire [7:0]dout;
```

```
// Unit Under Test port map
```

```
RegFile UUT (
```

```
    .ReadAddress(ra),
```

```
    .WriteAddress(wa),
```

```
    .WE(we),
```

```
    .DataIn(din),
```

```
    .DataOut(dout));
```

```
//continued on next slide
```

//testbench continued – stimulus for inputs

initial begin

we = 0;

ra = 4'b0000;

din = 8'd0;

for (wa = 4'h0; wa <= 4'hf; wa = wa + 1) begin //16 write operations

din = din + 5;

#5 we = 1;

//we pulse = 5ns

#5 we = 0;

//we period = 10ns

end

din = 8'd0;

//expected read-back value

for (ra = 4'h0; ra <= 4'hf; ra = ra + 1) begin

//read the 16 registers

din = din + 5;

//next value that was written

#10;

//read time 10ns

if (dout != din) \$display ("ERROR dout not correct. ");

end


\$finish;

end

endmodule

Producing a clock signal
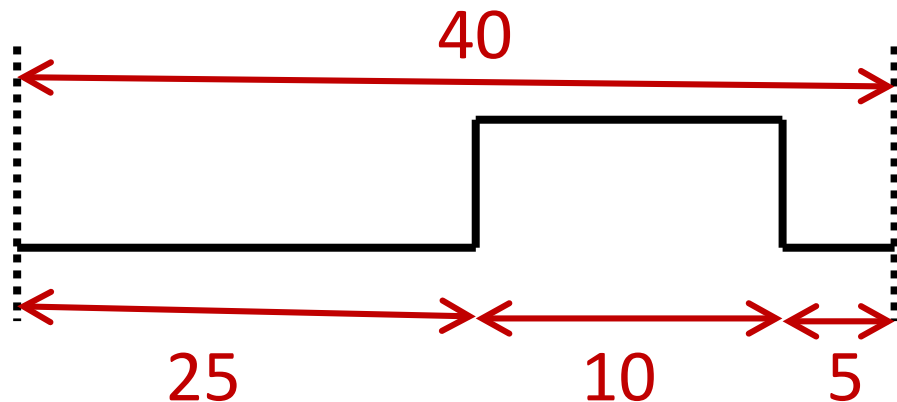
```
initial x = 0;           //set initial value
always begin             //block is repeated (assume t=0 initially)
    #25 x = 1;           //delay to t=25, then continue by assigning x=1
    #10 x = 0;           //delay to t=35, then continue by assigning x=0
    #5;                  //delay to t=40, then continue
end
```



Example – D flip flop

```
module example
```

```
    reg Q, Clk;
```

```
    wire D;
```

```
    assign D = 1;                                //D=1 for this example
```

```
    always @(posedge Clk) Q = D;                 //normal flip flop clocking
```

```
    initial Clk = 0;                             //initial state of Clk reg
```

```
    always #10 Clk = ~Clk;                       //toggle clock for period of 20
```

```
    initial begin
```

```
        #50;
```

```
        $finish; //simulation control – end simulation
```

```
    end
```

```
    always begin
```

```
        $display("T=“, %2g, $time,“ D=“, D,“ Clk =“, Clk,“ Q=“, Q); //generate output listing every 10 time units
```

```
        #10;
```

```
    end
```

```
endmodule
```

Verilog built-in primitive gates

- Verilog has 8 gate types that are primitive components:
and, or, nand, nor, xor, xnor, not, buf
- Format:
gate INSTANCE_NAME (Z,I1,I2,...IN); // list output first, followed by inputs

```
module carry_out(A,B,Cin,Cout)
  input A,B,Cin;
  output Cout;
  wire w1,w2,w3;
  and    A1 (w1,A,B);           //primitive and gate instances
  and    A2 (w2,A,Cin);
  and    A3 (w3,B,Cin);
  or     O1 (Cout,w1,w2,w3);    //primitive or gate instance
endmodule
```

Lists of assign/gate instance statements

- Can specify a comma-separated list of gates of one type
- Likewise for “assign” statements

```
module carry_out(A,B,Cin,Cout)
  input A,B,Cin;
  output Cout;
  wire w1,w2,w3,w4,w5;
  and   A1 (w1,A,B),           // list of three and gate instances
        A2 (w2,A,Cin),
        A3 (w3,B,Cin);
  assign w4 = w1 & w2,         // list of two assign statements
        Cout = w4 & w3;
endmodule
```

Specifying delays

- Net delays:

```
assign #8 a = b & c;    //a changes 8 time units after b/c change
wire #8 a = b & c;      //equivalent to the following statement pair
    wire a;
    assign #8 a = b & c;
//above also equivalent to the following statement pair
    wire #8 a;          //8 units of delay to any assignment to net a
    assign a = b & c;
```

Logic gate delays:

```
nand #5      N1(out1,in1,in2); //delay of 5 for any change at gate output
nand #(3,5)   N2(out2,in1,in2); //output rising delay=3, falling delay=5
nand #(3,5,7) N3(out3,in1,in2); //rising delay=3, falling delay=5, delay to hi-Z=7
```

Allow for process variations and loading

- Triplet of delay values: (minimum : typical : maximum)

// triplet of net delays

#(1.1 : 1.4 : 1.5) assign delay_a = a;

// triplet of nand gate rise, fall times

nand #(1:2:3, 2:3:4) N1(out1, in1, in2);

// 3 triplets of buffer delays, for rise, fall and change to hi-Z state

buf #(1:2:3, 2:3:4, 4:5:6) B1(out2, in3);

Specify block for pin-to-pin delays

```
module DFF (Q, clk, D, pre, clr);  
  input clk,D,pre,clr; output Q;  
  DFlipFlop(Q, clk, D) ; //previously-defined D flip flop module  
  specify specparam  
    tPLH_clk_Q = 3, tPHL_clk_Q = 2.9;  
    tPLH_set_Q = 1.2, tPHL_set_Q = 1.1;  
    (clk => Q) = (tPLH_clk_Q,tPHL_clk_Q); //=> clk to Q (rise,fall)  
    (pre,clr *> Q) = (tPLH_set_Q,tPHL_set_Q); //*> each input to each output  
end specify  
endmodule
```

Verilog simulation commands

\$finish //stop simulation

\$time //current simulation time

\$display("Some text to be printed to listing window");

\$monitor("T=", \$time, " A=", A, " B=", B); //print text & signals to list window

T=0 A=1 B=x //similar to C *printf* statement

T=5 A=0 B=1

...

\$dumpvars //

Signal strengths

- Verilog allows a signal strength to be associated with a logic state
(Similar to IEEE 1164 std_logic for VHDL)

Strength	Abbreviation	Value	Meaning
Supply	Su	7	Power supply
Strong	St	6	Default gate drive (default)
Pull	Pu	5	Pull up/down
Large	La	4	Large capacitance
Weak	We	3	Weak drive
Medium	Me	2	Medium capacitance
Small	Sm	1	Small capacitance
High Z	Hi	0	High impedance

Examples: *strong1, pull1, supply0, Su1, Su0, etc.*

User-defined primitive gates (combinational)

- Define own primitive “gates” via a truth table

```
primitive Adder (Sum, InA, InB);  
  output Sum; input InA, InB;  
  table  
    // inputs : output  
      00 : 0;  
      01: 1;  
      10: 1;  
      11 : 0;  
  endtable  
endprimitive
```

User-defined primitive gates (sequential)

- Include a “state” in the primitive truth table between input & output

```
primitive Dlatch (Q, Clock, Data);
```

```
  output Q; reg Q; input Clock, Data;
```

```
  table
```

```
    // inputs : present state : output (next state)
```

```
      1 0 : ? : 0 ;      // ? Represents 0, 1, or x
```

```
      1 1 : b : 1 ;      // b Represents 0 or 1 input
```

```
      1 1 : x : 1 ;      // can combine with previous line
```

```
      0 1 : ? : - ;      // - represents no change in output
```

```
  endtable
```

```
endprimitive
```