

TYPE OF QUESTION: MCQ


# Semi Design

find your way in #VLSI with us

No.of Questions : 10
 
## QUESTION 1:

The boolean function  $f$  implemented in the figure using two input multiplexes is :





- 
- A.  $A(\sim B)C + AB(\sim C)$
  - B.  $ABC + A\sim(BC)$
  - C.  $(\sim A)BC + \sim(ABC)$
  - D.  $(\sim AB)C + (\sim A)B(\sim C)$

**QUESTION 2:**


The digital block shown in the figure below is realized using 2 positive edge triggered flipflops. Assume that for  $t < t_0$ ,  $Q_1 = Q_2 = 0$ .

The circuit in the digital block is given by:

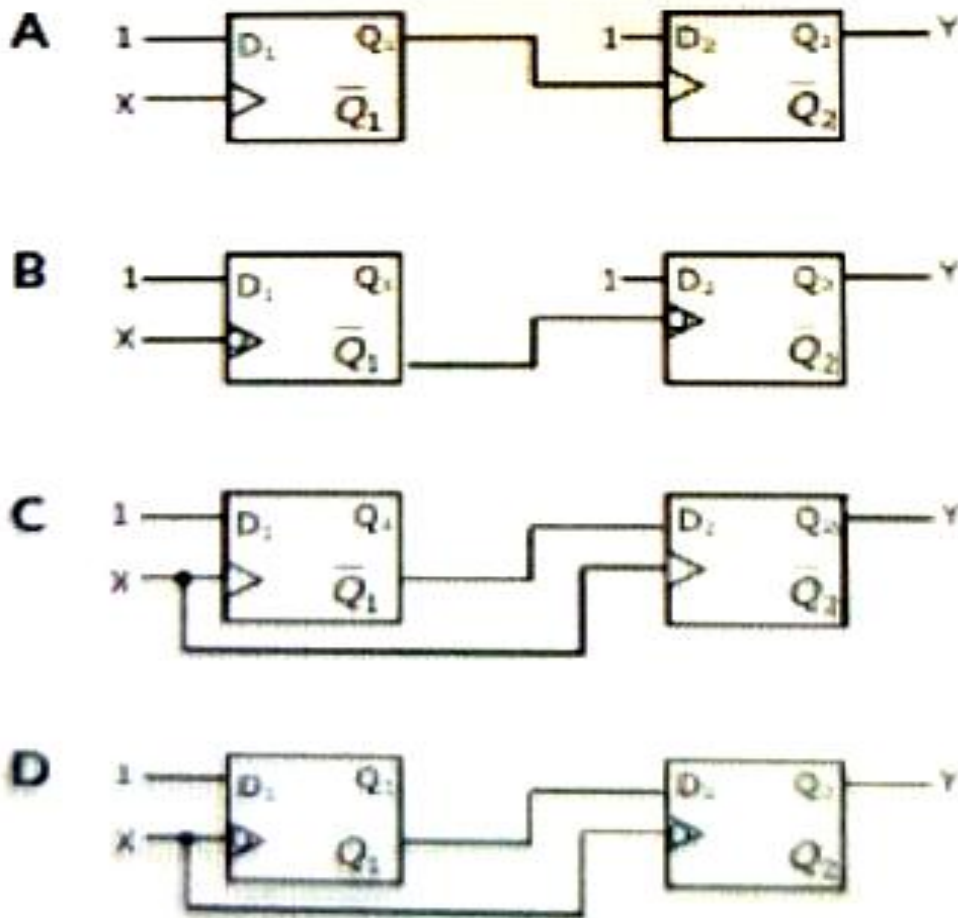 

 **QUESTION 3:**


In the following figure, if a net Y and W are being driven as shown, what is the resultant strength value on:



- E.  $\sim(AB(\sim C))$
- F.  $\sim A$
- G.  $AB(\sim C)$
- H. A

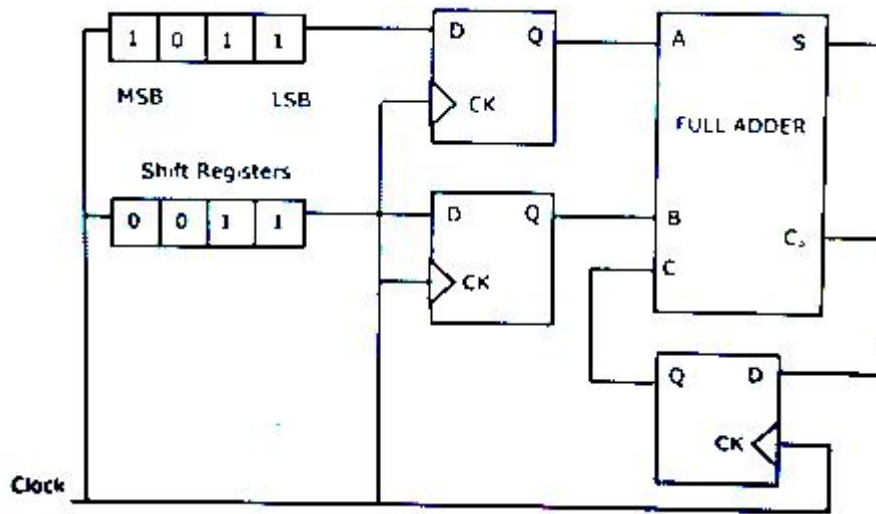**QUESTION 4:**

For the circuit shown in figure below, two parallel-in serial-out shift registers loaded with the data shown are used to feed the data to a full adder. Initially all the the flip flops are in clear state. After applying two clock cycles, the outputs of the full adder should be :



- I.  $S=0, C_0=0$
- J.  $S=0, C_0=1$
- K.  $S=1, C_0=0$
- L.  $S=1, C_0=1$

### QUESTION 5:

A boolean function  $f$  of two variables  $x$  and  $y$  is defined as follows :

$$f(0, 0) = f(0, 1) = f(1, 1) = 1; f(1, 0) = 0;$$

Assuming complements of  $x$  and  $y$  are not available, a minimum cost solution for realizing  $f$  using only 2-input NOR gates and 2-input OR gates (each having unit cost) would have a total cost

- M. 1 unit
- N. 4 units
- O. 3 units
- P. 2 units

**QUESTION 6:**

*Analyze the code segment and choose the right answer.*

```
module top;  
  
    assign out=a&b|c;  
  
    initial begin  
  
        #50 force out=a&b&c;  
        #50 release out;  
  
    end  
endmodule
```

- Q. Expression a&b&c is assigned to net from 50 to 100
- R. a&b&c overrides assignment of a&b|c completely throughout the simulation time
- S. All of the above
- T. None of the above

**QUESTION 7:**


*Analyze the code below and choose the right options?*

```
reg clock;
initial begin
  clock=1'b0;
  forever #10 clock=~clock;
end
```

- A. The forever loop will execute the statement infinitely
- B. Timing control construct is optional in forever
- C. All of the above
- D. None of the above

 **QUESTION 8:**

*A master slave flipflop has the characteristic that :*



- A. Change in the input immediately reflected in the output
- B. Change in the output occurs when the state of master is affected
- C. Change in the output occurs when the state of slave is affected

D. Both master and slave states are affected at same time

**QUESTION 9:**

*What is the order of execution of below code?*

```

    module zero;
    reg a,b,c;

    //initial block with zero delay

    initial
    begin
        #0 a=1;
        #0 b=1;
        #0 c=1;
        $display("zero delay control a=%b, b=%b, c=%b", a,b,c);
    end

    //initial block without zero dealy

    initial c=0;
    initial
    begin
        a=0;
        b=0;
        $display("zero delay control a=%b, b=%b, c=%b", a,b,c);
    end

endmodule

```

- A. zero dealy control statement is executed first
- B. zero dealy control statement is executed only after all other statements
- C. zero dealy control statement is non-deterministic
- D. None of the above

**QUESTION 10:**

*What is missing in top module of below code segment*

```
module my_verilog;  
parameter p1 = 5;  
initial $display("displaying my_verilog=%d",p1);  
endmodule
```

```
module top;  
defparam q1.p1=6,q2.p1=4;  
endmodule
```

- A. Initial statement
- B. One module instance of my\_verilog
- C. Two module instance of my\_verilog
- D. All of the above

\*\*\*\*\*END\*\*\*\*\*

Regd. No.- UP28D0036817 Address: D/203, Grand Forte Sigma IV, Greater Noida, Uttar Pradesh, India 201308 Contact: +91-9599745251 | +91-9958121220 | [www.semidesign.in](http://www.semidesign.in) | info@semidesign.in

-- Semi Design Team